

Chapter 19. Electric Circuit

Contents:

- 19.1 Circuit components
- 19.2 Combinations of resistors
- 19.3 Electrical safety

New word list:

Fuse Junction generator motor transformer relay
Mains electricity mains supply graphite short circuit open circuit closed circuit

4.3 Electric circuits

4.3.1 Circuit diagrams and circuit components

Core

- 1 Draw and interpret circuit diagrams containing cells, batteries, power supplies, generators, potential dividers, switches, resistors (fixed and variable), heaters, thermistors (NTC only), light-dependent resistors (LDRs), lamps, motors, ammeters, voltmeters, magnetising coils, transformers, fuses and relays, and know how these components behave in the circuit

Supplement

- 2 Draw and interpret circuit diagrams containing diodes and light-emitting diodes (LEDs), and know how these components behave in the circuit

4.3.2 Series and parallel circuits

Core

- 1 Know that the current at every point in a series circuit is the same

Supplement

- 8 Recall and use in calculations, the fact that:
 - (a) the sum of the currents entering a junction in a parallel circuit is equal to the sum of the currents that leave the junction
 - (b) the total p.d. across the components in a series circuit is equal to the sum of the individual p.d.s across each component
 - (c) the p.d. across an arrangement of parallel resistances is the same as the p.d. across one branch in the arrangement of the parallel resistances

- 2 Know how to construct and use series and parallel circuits
- 3 Calculate the combined e.m.f. of several sources in series
- 4 Calculate the combined resistance of two or more resistors in series
- 5 State that, for a parallel circuit, the current from the source is larger than the current in each branch
- 6 State that the combined resistance of two resistors in parallel is less than that of either resistor by itself
- 7 State the advantages of connecting lamps in parallel in a lighting circuit
- 9 Explain that the sum of the currents into a junction is the same as the sum of the currents out of the junction
- 10 Calculate the combined resistance of two resistors in parallel

4.3 Electric circuits continued

4.3.3 Action and use of circuit components

Core

- 1 Know that the p.d. across an electrical conductor increases as its resistance increases for a constant current

Supplement

- 2 Describe the action of a variable potential divider
- 3 Recall and use the equation for two resistors used as a potential divider

$$\frac{R_1}{R_2} = \frac{V_1}{V_2}$$


4.4 Electrical safety

Core

- 1 State the hazards of:
 - (a) damaged insulation
 - (b) overheating cables
 - (c) damp conditions
 - (d) excess current from overloading of plugs, extension leads, single and multiple sockets when using a mains supply
- 2 Know that a mains circuit consists of a live wire (line wire), a neutral wire and an earth wire and explain why a switch must be connected to the live wire for the circuit to be switched off safely
- 3 Explain the use and operation of trip switches and fuses and choose appropriate fuse ratings and trip switch settings
- 4 Explain why the outer casing of an electrical appliance must be either non-conducting (double-insulated) or earthed
- 5 State that a fuse without an earth wire protects the circuit and the cabling for a double-insulated appliance

Supplement


19.1 Circuit components

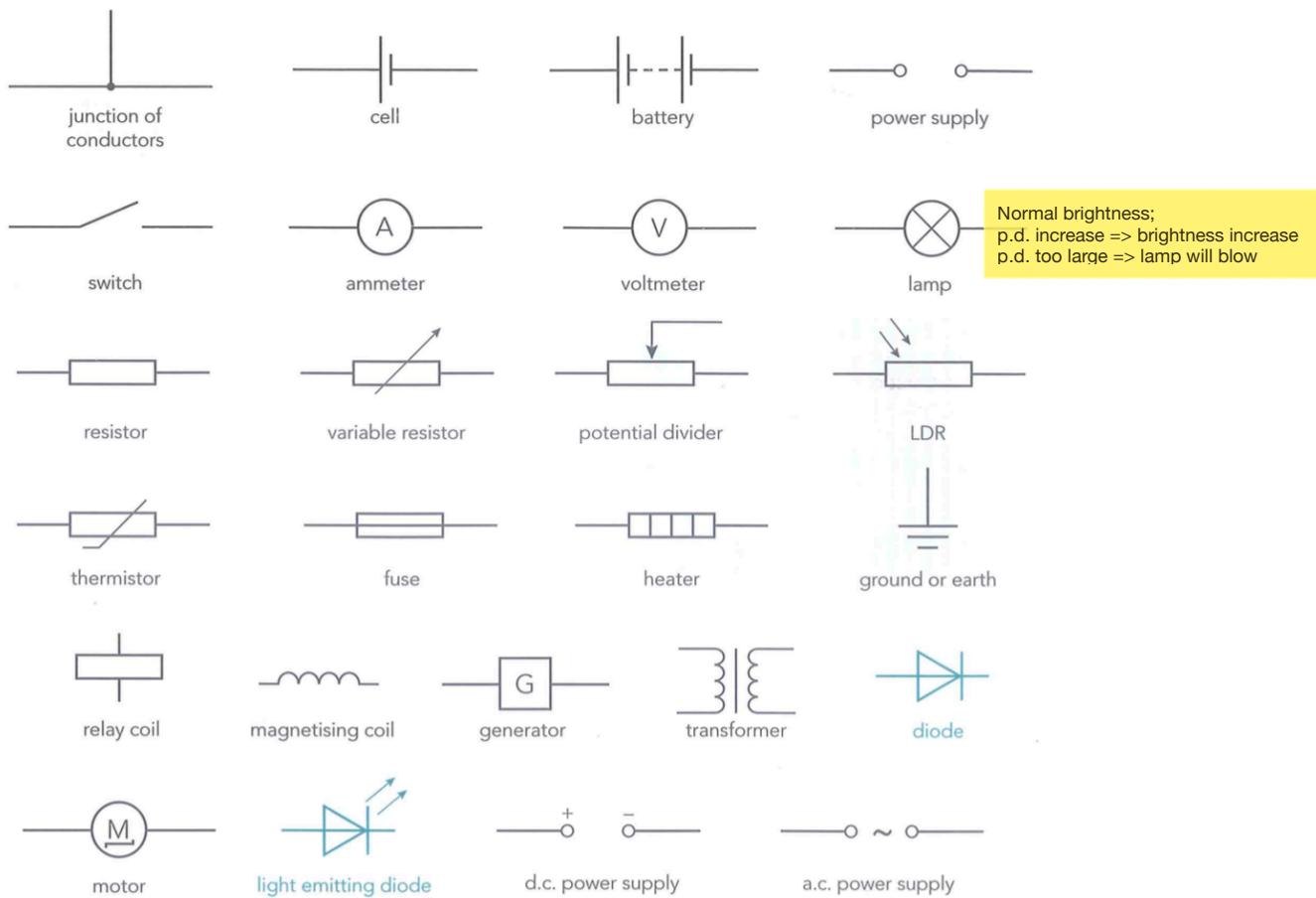



resistors & variable resistor




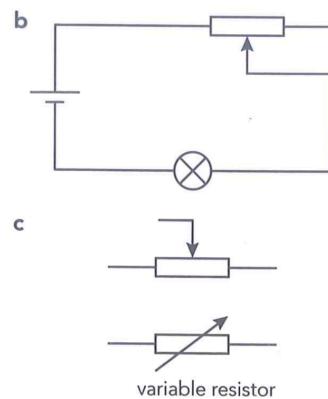
Resistor material: Metal(aluminum, copper, etc.), graphite




light-dependent resistor (LDR)

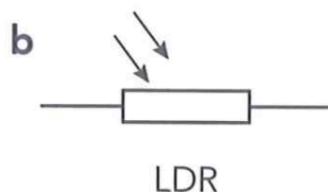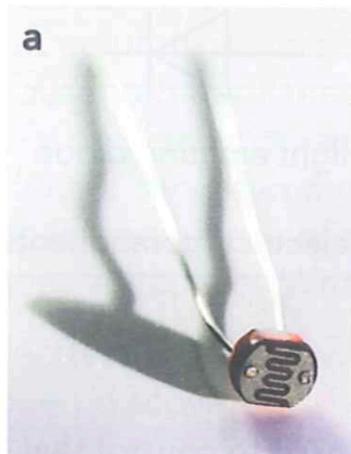




Thermistor

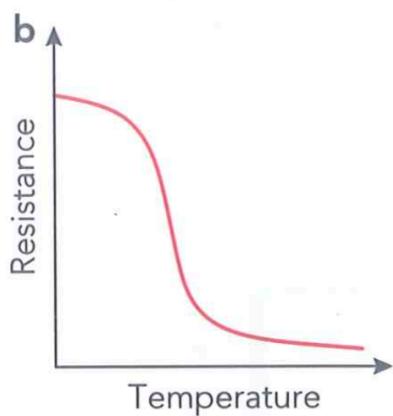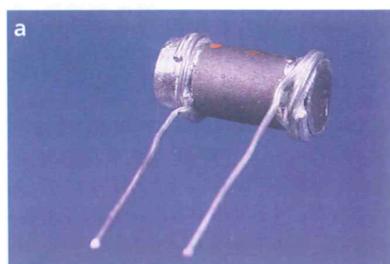

relay

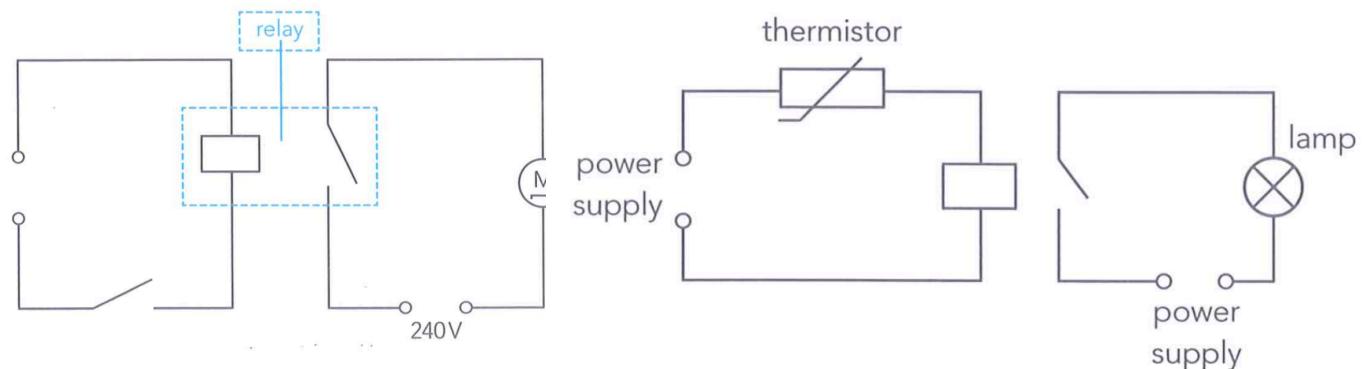


Diode & light-emitting diode (LED)

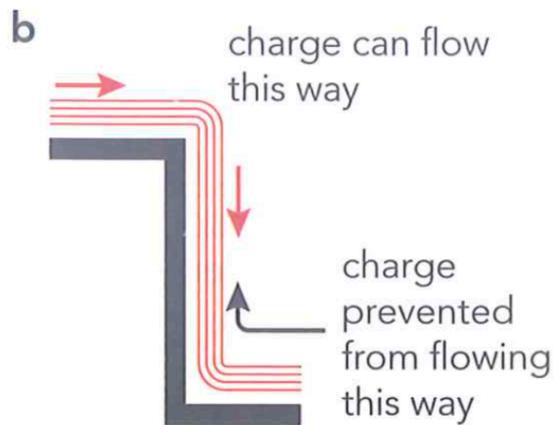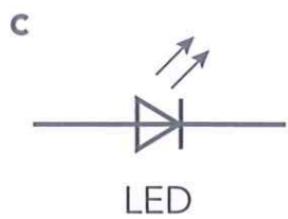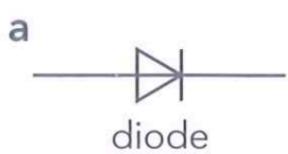


19.2 Combinations of resistors

Effective resistance: 等效电阻

Resistors in series:

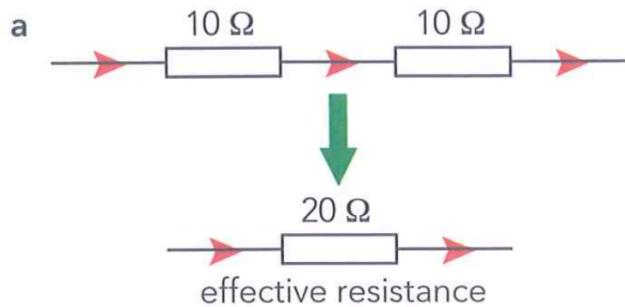
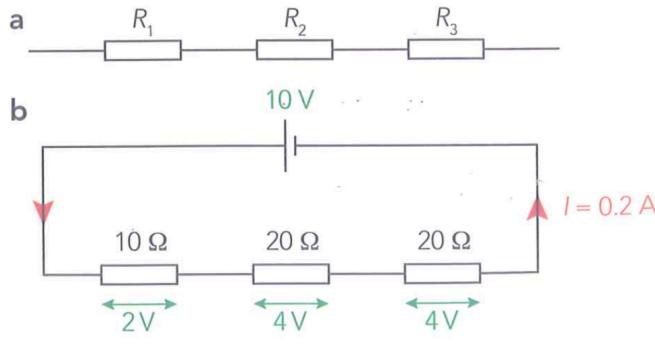
$$\text{Proof: } IR = V = V_1 + V_2 = IR_1 + IR_2 \Rightarrow R = R_1 + R_2$$



$$I = I_1 = I_2 \text{ (charge conservation)}$$

$$V = V_1 + V_2 \text{ (energy conservation)}$$

$$R = R_1 + R_2$$

$$V_1 = \frac{R_1}{R_1 + R_2} V$$

$$P = P_1 + P_2$$

Characteristics


- Always switched on/off at the same time;
- One breaks, others won't work;
- Share voltage

Exercise:

One 4 ohms resistor and one 6 ohms resistor are connected in a series circuit with a 6 V power supply. Calculate:

- 1, The combined resistance of the two resistors
- 2, The current that flows in the circuit
- 3, The p.d. across each resistor


Potential divider circuit

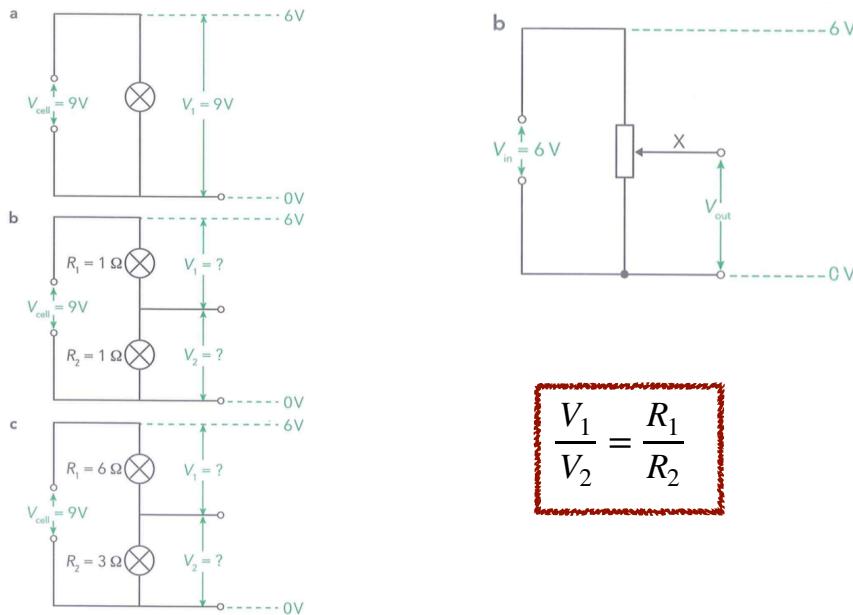


$$\boxed{\frac{V_1}{V_2} = \frac{R_1}{R_2}}$$

Exercise:

A potential divider circuit is required to produce an output voltage of 8V across a resistor, R1, of 600 ohms. The supply voltage is 12V. What is the required value of the series resistor, R2?

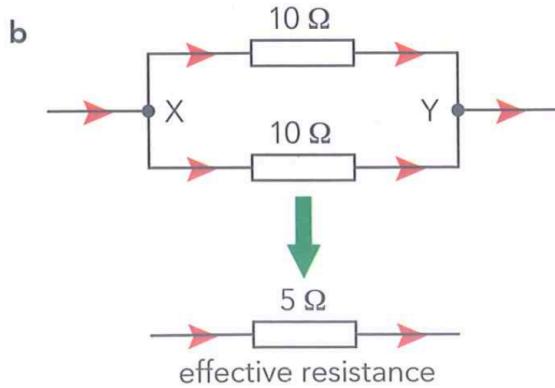Resistors in parallel:
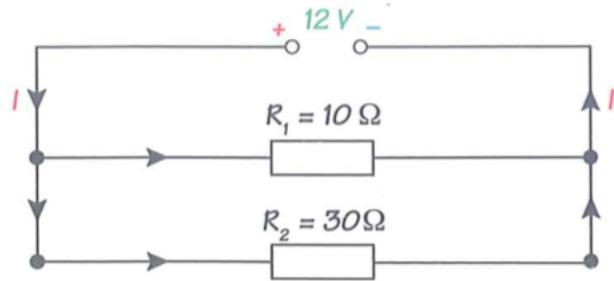
$$\text{Proof: } I = I_1 + I_2 \Rightarrow \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$\begin{aligned}I &= I_1 + I_2 \\V &= V_1 = V_2 \\ \frac{1}{R} &= \frac{1}{R_1} + \frac{1}{R_2} \\P &= P_1 + P_2\end{aligned}$$

Characteristics

- Can be switched on/off separately
- One breaks, others still work
- Can have full voltage

in particular:**N R in parallel:**

$$R_{tot} = \frac{R}{n}$$

Putting it all together:

Work out the current through, and the voltage across, each lamp in the circuit.

Summarize your result in the table below.

$$V_{AB} = e.m.f. = 9.0V = V_{CE}$$


$$I_{AB} = \frac{V_{AB}}{R_1} = 1.5A$$

$$R_{34} = R_3 + R_4 = 8\Omega$$


$$R_{CD} = 4\Omega$$

$$R_{CE} = 12\Omega \quad V_{CE} = 9.0V \quad I_{CE} = \frac{V_{CE}}{R_{CE}} = 0.75A = I_{DE}$$
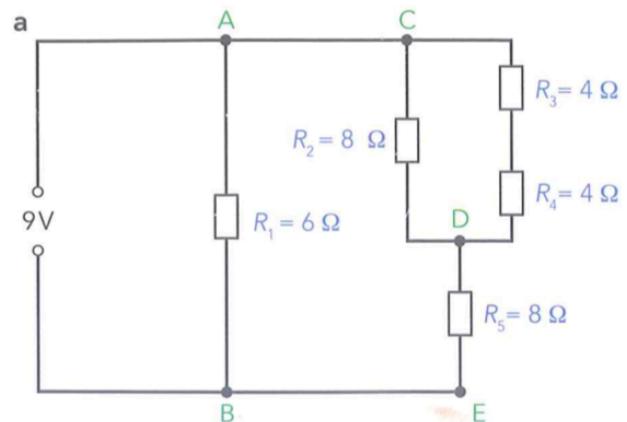
$$I_2 = I_3 = I_4 = \frac{I_{DE}}{2} = 0.375A$$



Resistor	Source	1	2	3	4	5
Voltage	9.0V	9.0V	3.0V	1.5V	1.5V	6.0V
Current	2.25A	1.5A	0.375A	0.375A	0.375A	0.75A


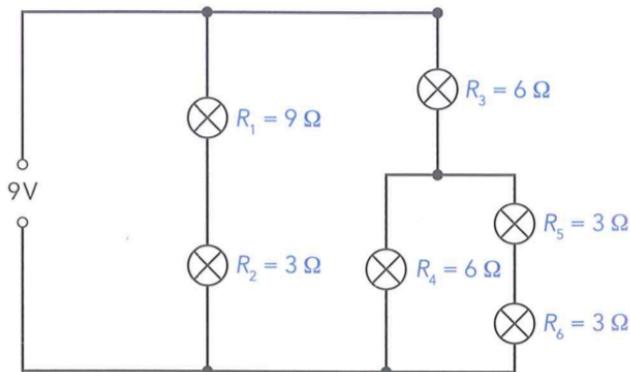
Exercise:

19.3 Electrical safety

Electrical hazards


Fire <= Overheating of wire, Excess current from overloading

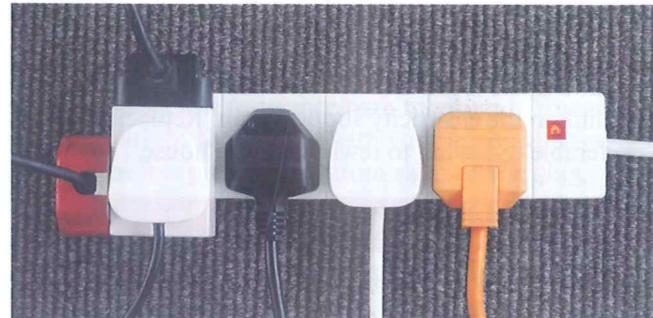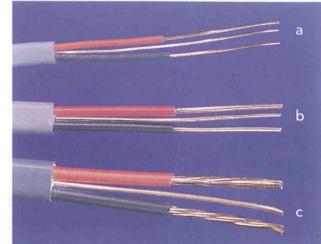Electrical shock <= Damaged insulation, Damp condition



Solutions:

1. Earthing

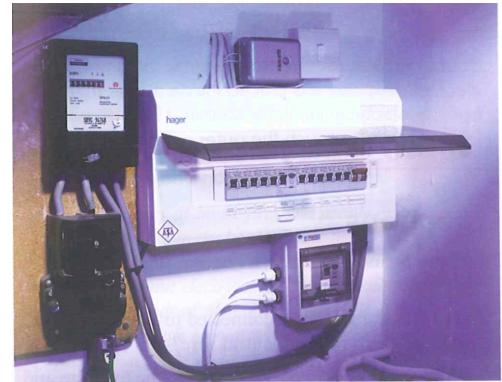

2. Use fuse / trip switch

3. Double insulation

